

## PreDP revision questions Answers for Section B of the exam

### Unit 5 and 6: Electricity and Electronics

- (a) (i) 0 (A) / zero Unit penalty if wrong unit B1
- (ii) 12 V B1
- (b) (i)  $V / R$  OR  $V = IR$  in any form, letters, words or numbers C1  
0.5 A A1
- (ii)  $8 \times$  candidate's (i) OR  $8/24 \times 12$  C1  
4 V OR 4.0 V e.c.f. A1
- (c)  $1/R_1 + 1/R_2 = 1/R$  OR  $R = R_1 R_2 / (R_1 + R_2)$  in any form B1  
 $5.3 (\Omega)$  OR  $5\frac{1}{3} (\Omega)$  OR  $16/3 (\Omega)$  C1  
12 / candidate's R C1  
2.25 A c.a.o. A1
- Alternatively:  $12/16 (= 0.75)$  OR  $12/8 (= 1.5)$  C1  
 $12/16 (= 0.75)$  AND  $12/8 (= 1.5)$  C1  
Currents added C1  
2.25 A c.a.o. A1 [10]

(a) A NOT or inverter B1  
 B AND B1

(b) (accept 1 or ON for HIGH, and 0 or OFF or NOT HIGH for LOW throughout)

(i) A – HIGH and B – LOW (both) no e.c.f. B1

(ii) A – HIGH and B – HIGH (both) no e.c.f. B1

(iii) A – LOW and B – LOW (both) no e.c.f. B1

(c) (i) B cannot provide enough power / current for lamp, or equiv.  
 OR allows remote lamp B1

(ii) the second one / dark and warm / HIGH, HIGH e.c.f. from (b) B1

(iii) warning if temperature in a closed / dark space (e.g. refrigerator, kiln) reaches too high a value  
 N.B. “to switch on a lamp when it is dark and warm” not accepted B1

[8]

(a) NOT or inverter B1

(b) (i) thermistor NOT thermal resistor B1

(ii) resistance increases OR voltage across it increases B1

(c) (i) LOW or 0 or off or NOT HIGH B1

(ii) (much) larger/ large / higher / high B1

(iii) low temperature e.c.f. from (c) (ii) B1

(d) to allow adjustment of the temp. at which relay will close / heater comes on B1

(e) automatic control or wtte of heating system / air-conditioning / automatic room heater  
 OR thermostat  
 OR any other sensible suggestion involving control of heating B1

[8]

(a) diode B1

(b) (i)  $2\ \Omega$  B1

(ii) 24 OR  $22 + 2\ (\Omega)$  seen C1

$$1/R = 1/R_1 + 1/R_2 (+ 1/R_3) \text{ OR } (R =) \frac{R_1 R_2}{R_1 + R_2}$$

seen or used with any 2 resistors

ignore extra resistance added to expression for R in equation C1

$6\ \Omega$  A1

(c) N.B. marks may be scored anywhere in (c)

(current =) zero / very small M1

diode reverse biased

OR polarity wrong OR facing wrong way

OR diode only conducts R / + to L / - A1

(d) use  $I = V/R$  OR  $P = VI$  OR  $P = V^2/R$  symbols, numbers or words M1

use of  $R = 8\ (\Omega)$  & correct calculation to give 2W

OR  $R = 4 / 0.5 = 8\ (\Omega)$  OR  $R = 4^2 / 2 = 8\ (\Omega)$

OR any other calculation(s) using ( $I = V/R$  &  $P = VI$ ) OR  $P = V^2/R$  to deduce  $8\ (\Omega)$  M1

switch position B (NOTE: this is dependent on both M1s being scored)

ignore any calculations using  $2\ \Omega$  A1 [10]

(a) **analogue** any reading possible/idea of continuous variation of value of quantity B1

**digital** idea of two states only B1

(b) if both inputs are 1/high, the output is 1/high only added to previous line B1

OR if either or both inputs are 0/low, then output is 0/low (accept both answers in form of a truth table) B1

(a) (E =) Pt symbols or numbers OR  $100 \times 13 \times 3600$  OR  $0.1 \times 13$   
 OR 3 960 000 OR 4 320 000 C1  
 4 680 000 J OR 4.68 MJ OR 1.3 kWh OR 1300 Wh A1

(b) EITHER

$I = P/V$  in any form OR  $P/V$  OR 100/250 OR 0.4 A C1

$Q = It$  OR  $0.4 \times 13 \times 3600$  OR candidate's current  $\times 13 \times 3600$   
 OR candidate's current  $\times$  candidate's time in s C1

18 720 C e.c.f. A1

OR

volts = joules/coulombs in any form C1

4680000/250 OR candidate's E/250 C1

18 720 C e.c.f. A1

(c) (lost as/changed to) heat/light OR lost to air/surroundings B1

(a) increases (as current increases) M1  
 at an increasing rate A1

(b) (i)  $25 \Omega$  B1

(ii)  $IR$  in any form OR  $0.070 \times 25$  C1  
 1.7/1.8 V A1


(iii)  $(P =) IV$  OR  $I^2R$  OR  $V^2/R$  in any form, numbers, symbols or words C1  
 0.12 W e.c.f. from (i)/(ii) A1

(c) (i) answer to (b)(ii) B1

(ii) use of  $1/R = 1/R_1 + 1/R_2$  OR  $R = R_1R_2/(R_1 + R_2)$  C1  
 12.5  $\Omega$  A1

- (a) energy supplied / work done (per unit charge) to drive charge round a (complete) circuit B1  
 OR B1  
 p.d. / voltage across battery / power source B1
- (b) (i)  $P = IV$  OR  $(I =) P/V$  OR  $(I =) 60/240$  C1  
 $= 0.25 \text{ A}$  OR  $\frac{1}{4} \text{ A}$  A1
- (ii)  $I = V/R$  OR other version OR  $(R =) V/I$  C1  
 OR  $(R =) 240/0.25$   
 OR  $P = V^2/R$  or other version e.g.  $(R =) V^2/P$   
 OR  $(R =) 240^2/60$   
 $R = 960 \Omega$  A1
- (c) current in series circuit  $= 240 / 972 = 0.247 \text{ A}$  B1
- current suits both bulbs, (so both light up so Y is correct) B1  
 OR  
 p.d. across bulb A  $= 240 \times (960/972) = 237 \text{ V}$   
 p.d. across bulb B  $= 240 \times 12/972 = 2.96 \text{ V}$  B1  
 p.d. suits both bulbs, (so both light up so Y correct) B1 [8]

- (a) correct symbol for OR gate

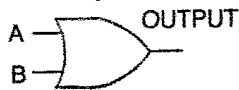

B1

- (b) output is low / zero / off if both inputs are low / zero / off B1

output is high / one / on if one input is high / one / on  
 BUT this mark is not scored if candidate puts output low when both inputs high B1

- (c) switches in doors are on if doors are open or vice versa B1  
 (switches in) doors provide inputs (to gate) B1  
 output (of gate) is connected to buzzer / warning light / alarm B1 [6]

- (a) (i) 4 V B1  
(ii) 12 V B1
- (b) (i)  $6\Omega$  B1  
(ii)  $1/R = 1/3 + 1/6$  OR  $(3 \times 6)/(3 + 6)$  C1  
 $2\Omega$  A1
- (c)  $V/R$  OR  $12/\text{candidate's (ii)}$  C1  
6 A ecf A1
- (d) (i) stays same B1  
(ii) decreases B1 [9]

- (a) (i) 1. resistance is constant / doesn't vary B1  
2. resistance increases B1  
(ii) 7 V B1
- (b) resistance of resistor =  $4/2.6$  (=  $1.54\Omega$ ) C1  
resistance of lamp =  $4/3.6$  (=  $1.11\Omega$ ) C1  
 $1/R = 1/R_1 + 1/R_2$  OR  $(R =) R_1 R_2 / (R_1 + R_2)$  OR either eq. with numbers C1  
 $0.645$  or  $0.65\Omega$  A1  
OR  
current through resistor = 2.6 A (C1)  
current through lamp = 3.6 A (C1)  
total current =  $2.6 + 3.6 = 6.2$  A (C1)  
 $0.645\Omega$  OR  $0.65\Omega$  OR  $R = 4/\text{sum of candidate's currents}$  (A1) [7]  
accept  $R$  value based on no. of sig. figs. for resistors used by candidate

- (a) decreases / low / very low / zero B1 [1]
- (b) (i) ecf from (a), both answers must be consistent with candidate's (a) B1  
 e.g. decreases / low / very low / zero increases / high / v. high / > 5V  
 light high OR 1 light low OR 0  
 AND dark low OR 0 AND dark high OR 1
- (ii) switch position P high OR 1  
 AND switch position Q low OR 0 B1 [2]
- (c) AND gate B1 [1]
- (d) transistor B1 [1]
- (e) any 2 of:  
 (input) A high  
 (input) B high  
 C high  
 transistor switches on/works  
 yes / it would work M1  
 A1 [2]

(a) (i) $I_1 = I_2 + I_3$	B1
(ii) $I_1 = I_4$ OR same	B1
(b) (i) $(V = IR = 0.80 \times 3.0 =) 2.4 \text{ V}$	A1
(ii) $I = V/R$ in any algebraic form OR $2.4 / 2$ OR (b)(i) / 2 OR any voltage divided by 2	C1
$(I_3 = V/R = 2.4 / 2 =) 1.2 \text{ A}$	A1
OR	
$I_3/I_2 = 3/2$	(C1)
$I_3 = 3/2 \times 0.8 \text{ A} = 1.2 \text{ A}$	(A1)
(iii) $(I_2 + I_3$ OR Current through $R = 0.8 + 1.2) = 2.0 \text{ (A)}$ OR $6 \text{ V} / 2 \text{ A}$ used	C1
Parallel combination formula: $1/r = 1/r_1 + 1/r_2$	
OR $(r =) r_1 r_2 / (r_1 + r_2)$	C1
Use of formula: combined resistance = $1.2 (\Omega)$	C1
$(R + 1.2 = 6/2 = 3.0 \Omega \quad R =) 1.8 \Omega$	A1
OR	
Current through $R = 0.8 + 1.2 = 2.0 \text{ (A)}$	(C1)
P.D. across $R = 6.0 - 2.4$	(C1)
$= 3.6 \text{ (V)}$	(C1)
$R = 3.6 / 2.0 = 1.8 \Omega$	(A1)

for (b) and (d) accept HIGH/LOW or ON/OFF

(a) NOR	B1	[1]
(b) outputs 1, 0, 0, 0 lose 1 mark e.e.o.o.	B2	[2]
(c) (i) OR and NOT gates either order	B1	
(ii) both symbols correct	B1	
OR <u>then</u> NOT, connected	B1	[3]
(d) logic level at Y, 0	B1	
logic level at Z, opposite to candidate's answer to Y	B1	[2]



(a) Transistor	B1	
(b) Resistor / variable resistor / rheostat identified	B1	
Light-dependent resistor / LDR identified	B1	
Resistor or alternative in gap A; LDR in gap B	B1	
(c) Thermistor / thermal resistor / heat or temperature dependent resistor identified	B1	
Thermistor (or alternative name) in gap A <u>and</u> resistor in gap B	B1	
(a) in order downwards: 1 1 1 0 c.a.o.	B1	
(b) (i) 1 AND 0 (e.c.f. from (b)(i))	B1	
(ii) NOT (gate) ( <b>allow</b> NOR (gate))	B1	
(c) R = 1 AND S = 0 (e.c.f. from (b)(i))	B1	
T = 1	B1	[5]
(a) (i) input high/on/1, output low/off/0 input low/off/0, output high/on/1 OR reverses/inverts state of input OR output opposite to input	B1	
(a) (ii) resistance changes as temperature changes	B1	
(i) at low temperature resistance of thermistor is high OR when temperature falls resistance of thermistor rises p.d. across thermistor is high OR p.d. across R is low (voltage) input to gate is low output of gate is high (and warning light is on)	B1 B1 B1 B1	
(ii) changes the temperature/set value at which the lamp comes on	B1	

- |     |   |  |   |                                |        |
|-----|---|--|---|--------------------------------|--------|
| (a) | row 1   | 0  | 0 | accept low / off               | B1     |
|     | row 2   | 0  | 1 | accept low / off and high / on | B1     |
|     | row 3   | 1  | 1 | accept high / on               | B1     |
|     |   |  |   |                                |        |
| (b) | 2 wires to flat (input) side, 1 wire from curved (output) side<br>do not accept pointed curved side or small circle   |  |   |                                | B1     |
|     |   |  |   |                                |        |
| (c) | NOT gate connected to output of AND gate<br>accept labelled boxes for gates<br>do not allow any extra gates or inputs |  |   |                                | M1     |
|     | NOT gate correct way round  |  |   |                                | A1     |
|     |   |  |   |                                |        |
| (a) | (i)   | 1. signal has same variation (with time) as the data   |   |                                | B1     |
|     |   | 2. consists of (a series of) 'highs' and 'lows'  |   |                                | B1     |
|     |   | <i>either</i> analogue is continuously variable (between limits)   |   |                                |        |
|     |   | <i>or</i> digital has no intermediate values   |   |                                | B1 [3] |
|     | (ii)  | e.g. can be regenerated / noise can be eliminated<br>extra data can be added to check / correct transmitted signal<br>(any two reasonable suggestions, 1 each) |   |                                | B2 [2] |